

Final Project

SAR ADC

Table of Contents

| | |
|--|----|
| Part 1: SAR Logic..... | 3 |
| 3) Report transient simulation results for the ring counter output, the code register output, and the EOC signal | 3 |
| Part 2: Transmission Gate..... | 6 |
| Part 3: Bottom-Plate Switch | 6 |
| Part 4: SAR ADC Design | 7 |
| Part 5: DC Functional Test | 8 |
| Part 6: Sine Wave Test | 11 |
| Part 7: Fully-Differential SAR ADC | 13 |
| Sine wave test..... | 14 |

Table of Figures

| | |
|---|----|
| Figure 1: 8-bit SAR logic schematic | 3 |
| Figure 2: 8-bit SAR logic testbench..... | 3 |
| Figure 3: SAR transient signals in all zeros case | 4 |
| Figure 4: SAR transient signals in all ones case | 4 |
| Figure 5: SAR transient signals in alternating zeros and ones case | 5 |
| Figure 6: Transmission gate schematic | 6 |
| Figure 7: Bottom-plate switch schematic..... | 6 |
| Figure 8: 8-bit capacitive DAC schematic | 7 |
| Figure 9: 8-bit SAR ADC schematic..... | 7 |
| Figure 10: 8-bit SAR ADC testbench | 8 |
| Figure 11: Transient waveforms in the V_{REFN} case | 8 |
| Figure 12: Transient V_{SAH} , V_{SAR} & V_{DAC} in the V_{REFN} case..... | 9 |
| Figure 13: Transient waveforms in the $V_{REFN} + (128+32+8+2+0.5)*V_{LSB}$ case..... | 9 |
| Figure 14: Transient V_{SAH} , V_{SAR} & V_{DAC} in the $V_{REFN} + (128+32+8+2+0.5)*V_{LSB}$ case..... | 10 |
| Figure 15: Transient waveforms in the V_{REFP} case..... | 10 |
| Figure 16: Transient V_{SAH} , V_{SAR} & V_{DAC} in the V_{REFP} case | 11 |
| Figure 17: Transient V_{in} & V_{sah} | 11 |
| Figure 18: V_{SAH} spectrum..... | 12 |
| Figure 19: Differential 8-bit SAR ADC schematic | 13 |
| Figure 20: Differential 8-bit SAR ADC testbench..... | 13 |
| Figure 21: Transient V_{in} and V_{SAH} | 14 |
| Figure 22: V_{SAH} spectrum in the differential topology..... | 14 |

Tables

Table 1: SAR logic table 5

Table 2: SAR specs 12

Table 3: SAR specs 15

Part 1: SAR Logic

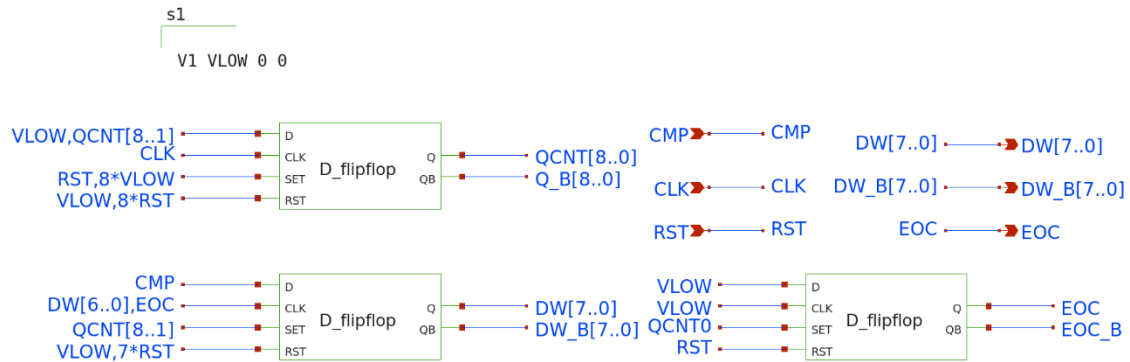


Figure 1: 8-bit SAR logic schematic

 


Figure 2: 8-bit SAR logic testbench

3) Report transient simulation results for the ring counter output, the code register output, and the EOC signal

- CMP is all zeros

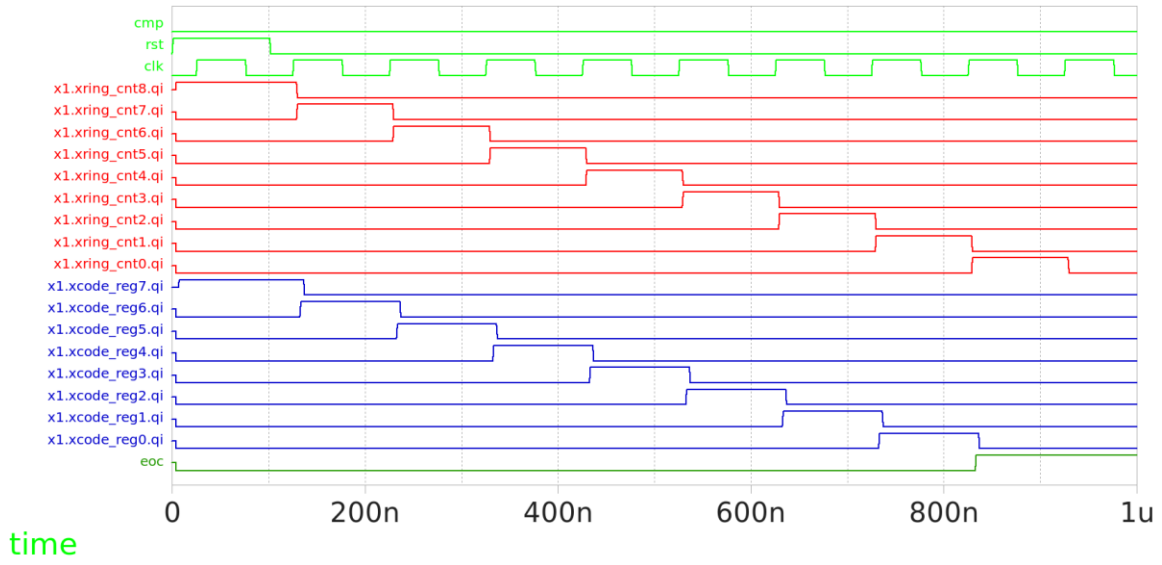


Figure 3: SAR transient signals in all zeros case

b. CMP is all ones

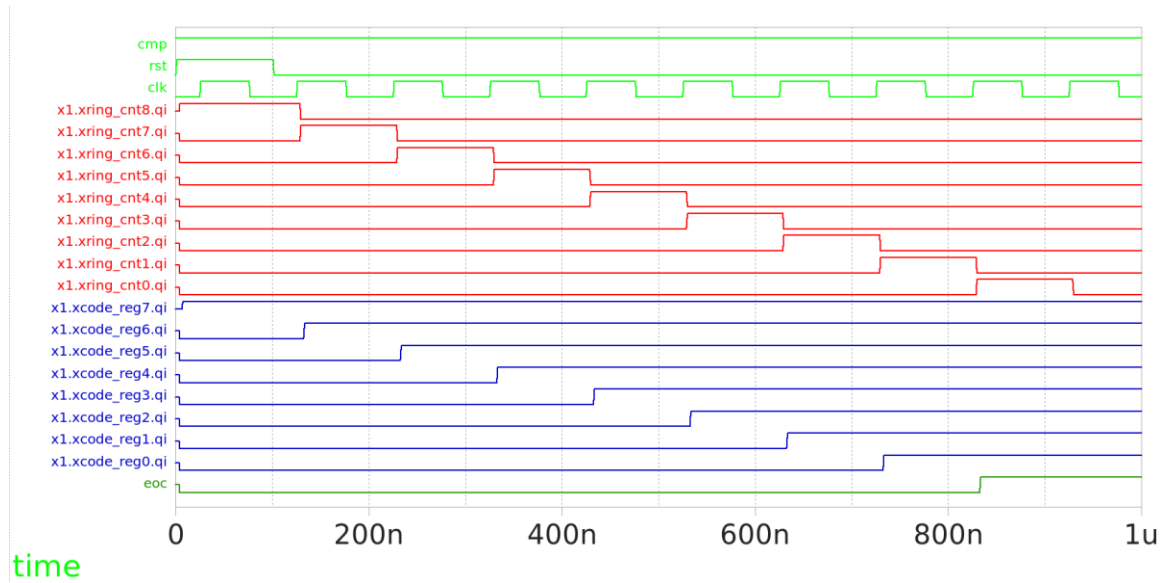


Figure 4: SAR transient signals in all ones case

c. CMP is alternating ones and zeros

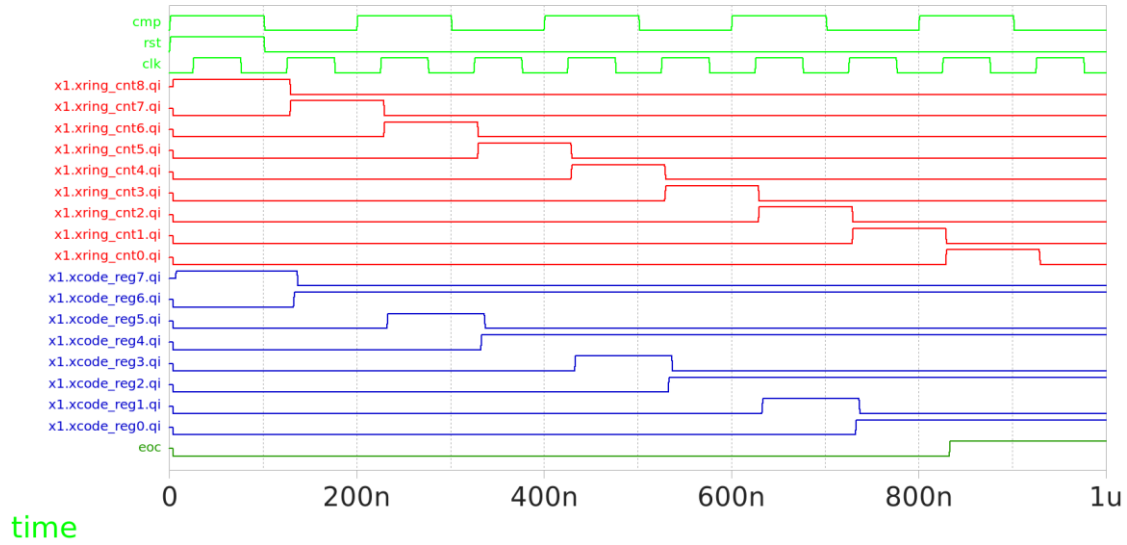


Figure 5: SAR transient signals in alternating zeros and ones case

The SAR logic implementation works as follows:

At first, the reset (RST) – which will be the start of conversion (SOC) i.e. the sampling clock – resets the end of conversion (EOC), the least 8 significant bits (LSBs) in the ring counter and the least 7 significant bits in the code register/digital output, and sets the most significant bit (MSB) in the ring counter so the ring counter starts with (100000000) and counts with the clock (CLK) where the 8 MSBs are the set for the code register so the digital output will be (100000000) which will be converted by the Digital to Analog converter (DAC) and compared by the comparator to the input and gives output CMP which is the D input to the code register which are synchronized by the 7 LSBs in the code register and the EOC. The next clock counts (010000000) in the ring counter so it sets DW[6] (digital word of the code register) to 1 which in turn is the CLK of DW[7] so the DW[6] positive edge transfers the CMP signal of the first comparison to DW[7] which is referred as B_7 in **Table 1**. The code register output ($B_71000000$) is converted and compared to the input giving new CMP signal and the next cycle the ring counter counts (001000000) and DW[5] is set to 1 which is the clock of DW[6] so DW[6] will be B_6 (the second cycle CMP signal) and so on till the ring counter counts 000000001 which sets the EOC to 1 which in turn is the CLK of DW[0] so it sets DW[0] to B_0 and so, the digital output is ready to be read from the code register output at the positive edge of the EOC. So, it successfully implements the SAR algorithm.

Table 1: SAR logic table

| Clock cycle | DW<7> | DW<6> | DW<5> | DW<4> | DW<3> | DW<2> | DW<1> | DW<0> | CMP |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1 (reset) | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | |
| 2 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | B_7 |
| 3 | B_7 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | B_6 |
| 4 | B_7 | B_6 | 1 | 0 | 0 | 0 | 0 | 0 | B_5 |
| 5 | B_7 | B_6 | B_5 | 1 | 0 | 0 | 0 | 0 | B_4 |
| 6 | B_7 | B_6 | B_5 | B_4 | 1 | 0 | 0 | 0 | B_3 |
| 7 | B_7 | B_6 | B_5 | B_4 | B_3 | 1 | 0 | 0 | B_2 |
| 8 | B_7 | B_6 | B_5 | B_4 | B_3 | B_2 | 1 | 0 | B_1 |
| 9 | B_7 | B_6 | B_5 | B_4 | B_3 | B_2 | B_1 | 1 | B_0 |
| 10 | B_7 | B_6 | B_5 | B_4 | B_3 | B_2 | B_1 | B_0 | EOC |

Part 2: Transmission Gate

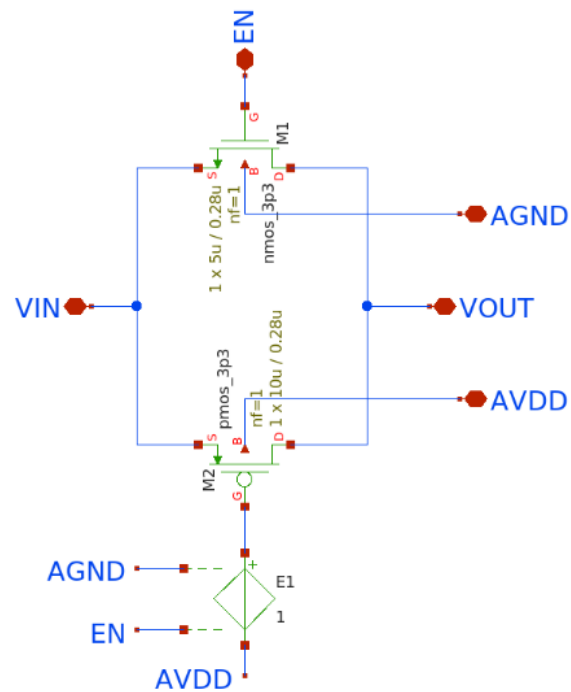


Figure 6: Transmission gate schematic

Part 3: Bottom-Plate Switch

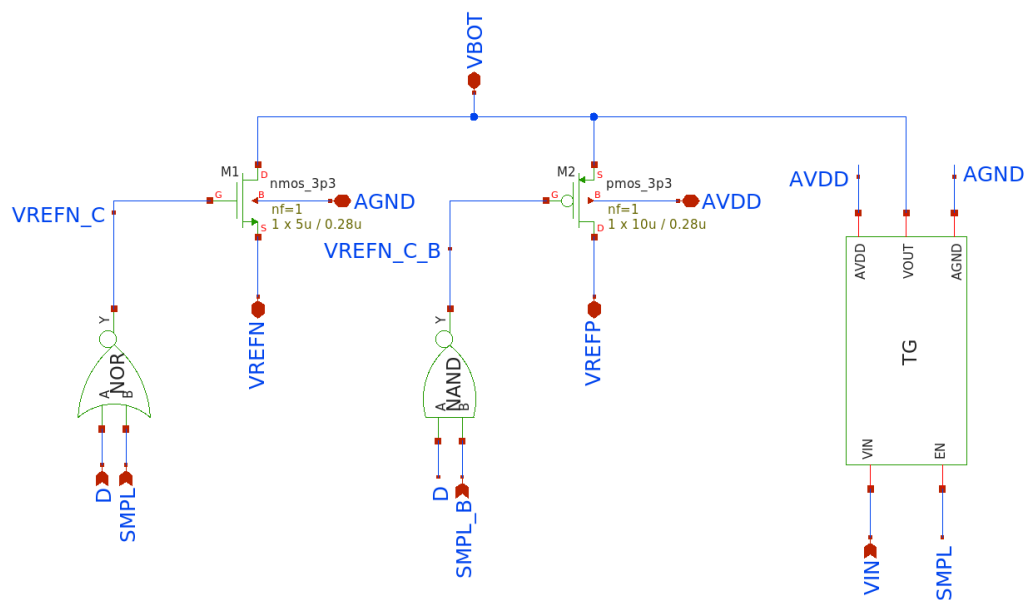


Figure 7: Bottom-plate switch schematic

Part 4: SAR ADC Design

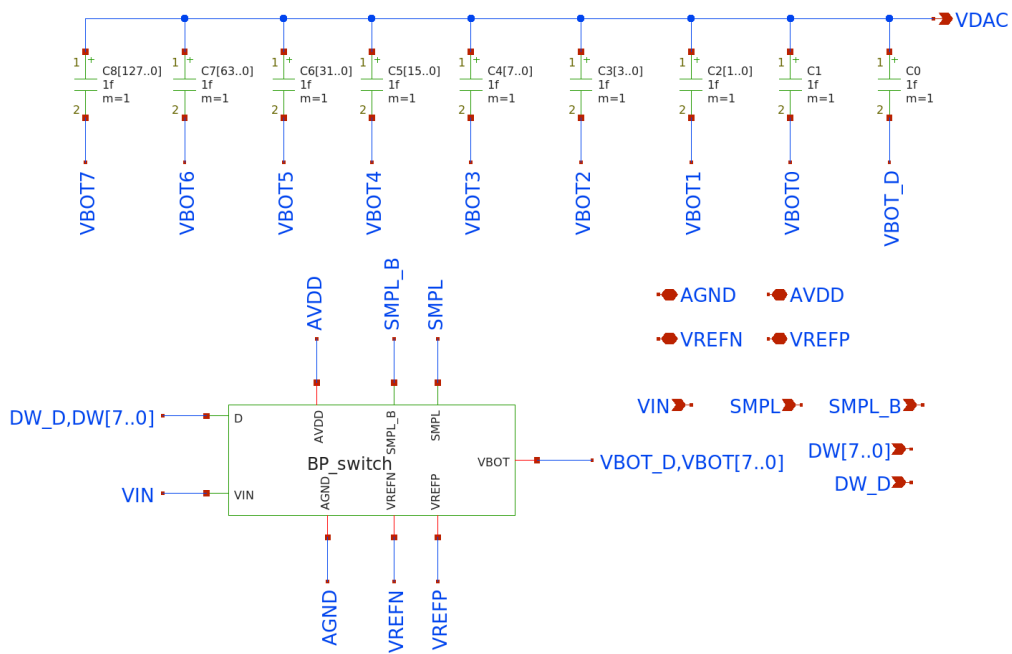


Figure 8: 8-bit capacitive DAC schematic


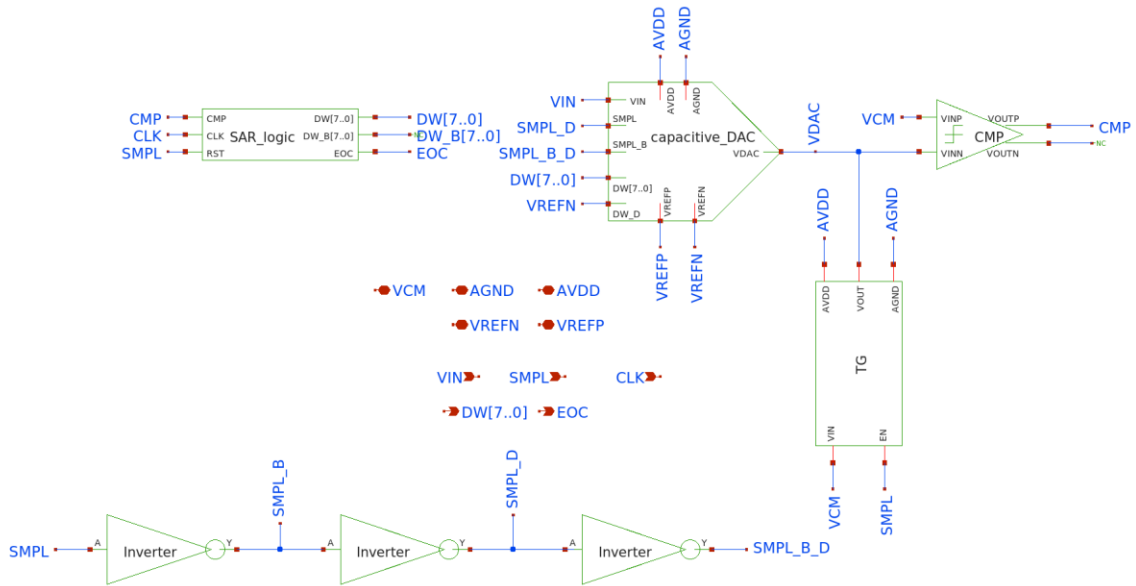


Figure 9: 8-bit SAR ADC schematic

 

a. $V_{IN} = V_{REFN}$



 


Figure 12: Transient V_{SAH} , V_{SAR} & V_{DAC} in the V_{REFN} case

b. $V_{IN} = V_{REFN} + (128+32+8+2+0.5)*V_{LSB}$

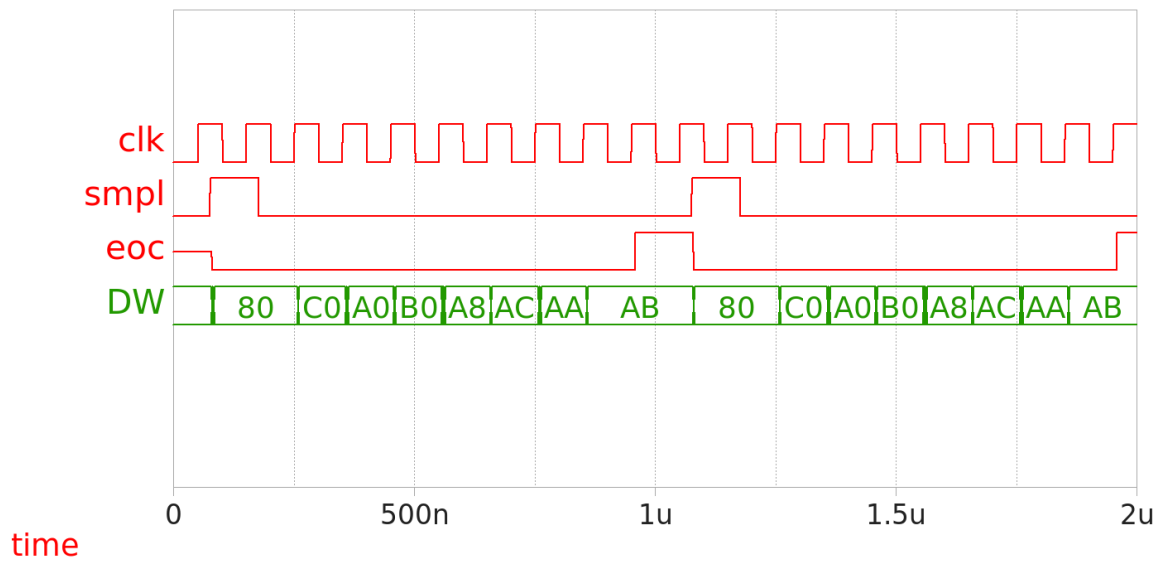


Figure 13: Transient waveforms in the $V_{REFN} + (128+32+8+2+0.5)*V_{LSB}$ case

 


Figure 14: Transient V_{SAH} , V_{SAR} & V_{DAC} in the $V_{REFN} + (128+32+8+2+0.5)*V_{LSB}$ case

c. $V_{IN} = V_{REFP}$

 


Figure 15: Transient waveforms in the V_{REFP} case

 


Figure 16: Transient V_{SAH} , V_{SAR} & V_{DAC} in the V_{REFP} case

The SAR DC functionality is good and the SAR works in a correct way as it compares with the analog value of (10000000) and the comparison decides the MSB then switches to the next bit and compares and so on.

Part 6: Sine Wave Test

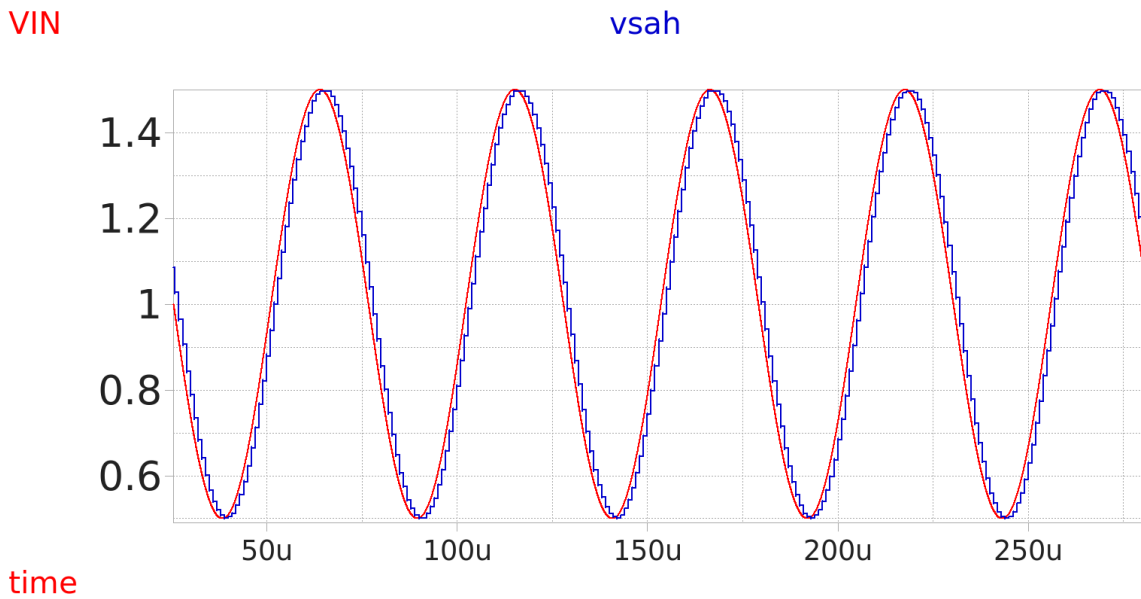


Figure 17: Transient V_{in} & V_{sah}

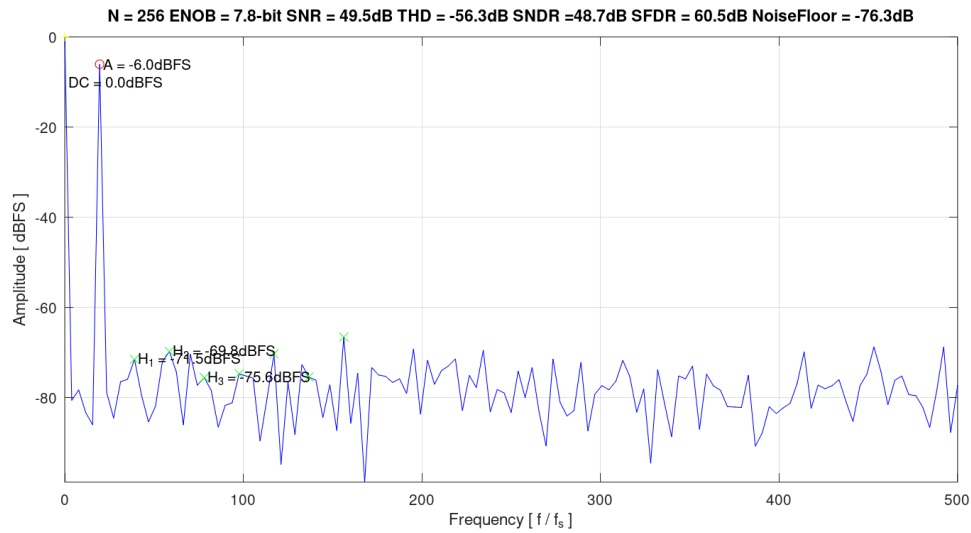


Figure 18: V_{SAH} spectrum

Table 2: SAR specs

| Spec | 8-bit SAR |
|--------------|-----------|
| ENOB | 7.8 bits |
| SINAD | 48.7 dB |
| SNR | 49.5 dB |
| SFDR | 60.5 dB |
| THD | -56.3 dB |
| Signal power | -6 dB |
| DC power | 0 dB |

- The ENOB is less than 8 due to the quantization error, pedestal step errors (clock feedthrough and charge injection) and may be also parasitics error.
- The noise are thermal noise and also quantization noise which are approximated to white noise as the test is coherent and the resolution is relatively high (huge number of levels) and the distortion is from the system non-linearities as the non-linear parasitics and the comparator non-linearity.
- The pedestal step errors are linear due to the bottom plate sampling so it enhances the total harmonic distortion.
- The signal amplitude is 0.5V and the power is evaluated as $20 \log(\text{Amplitude})$ not $20 \log \text{RMS}$ so its value is -6 dB.
- The DC value is 1V so it's 0 dB.

Part 7: Fully-Differential SAR ADC

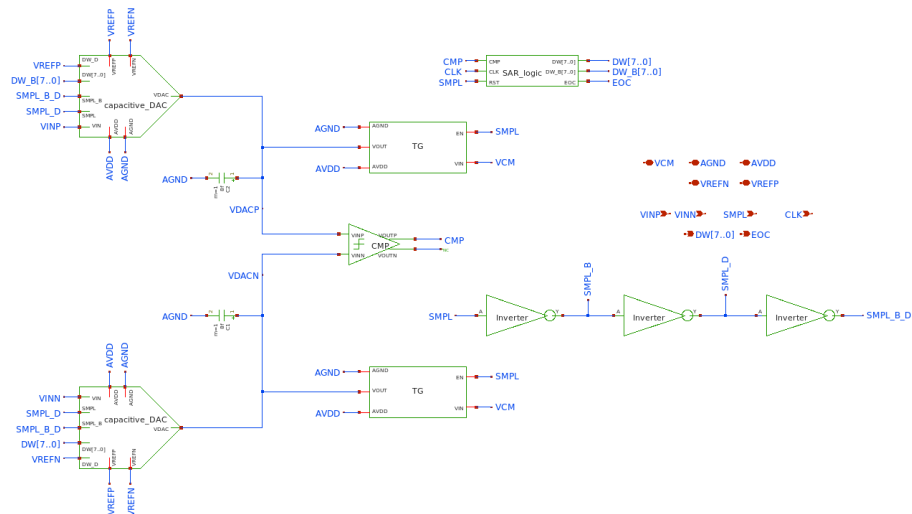


Figure 19: Differential 8-bit SAR ADC schematic

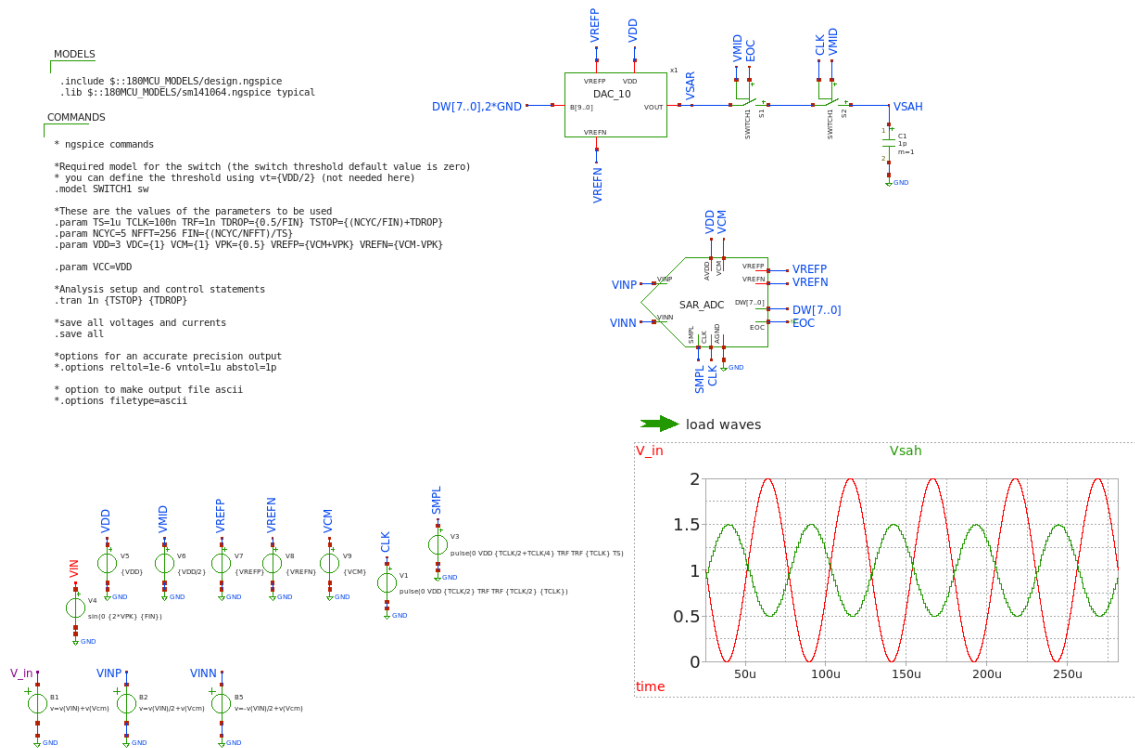


Figure 20: Differential 8-bit SAR ADC testbench

Sine wave test

 


Figure 21: Transient V_{in} and V_{SAH}

 


Figure 22: V_{SAH} spectrum in the differential topology

Table 3: SAR specs

| FOC | 8-bit SAR | Differential 8-bit SAR |
|------------------|----------------------------|--------------------------|
| ENOB | 7.8 bits | 7.8 bits |
| SINAD | 48.7 dB | 48.8 dB |
| SNR | 49.5 dB | 49.3 dB |
| SFDR | 60.5 dB | 60.6 dB |
| THD | -56.3 dB | -58.5 dB |
| Signal power | -6 dB | -6 dB |
| DC power | 0 dB | 0 dB |
| Highest harmonic | 2 nd = -69.8 dB | 3 rd = -72 dB |

- The only difference between the differential and single-ended is the larger input signal swing and the linearity enhancement as the differential removes the even harmonics in the capacitive DAC so, there are small differences in SINAD, SFDR and THD.
- The enhancement would be larger if it was fully-differential as it would enhance the linearity of the whole system (the whole SAR ADC) but in the current case the other system components non-linearities still exist (e.g. the comparator) and adds more parasitics, noise and pedestal step errors to the system as there are more switches which generate thermal noise and adds linear errors by bottom plate switches. The enhancement would be better at higher full scale too as the non-linearities would increase in the single-ended and the differential will remove the even harmonics.
- The DC power is not removed as the V_{SAH} output is single-ended and the SAR ADC is not fully-differential while the second harmonic is attenuated and now the third harmonic is the highest harmonic component.
- The differential signal amplitude is 1V to use the full scale in each terminal in the differential SAR (from V_{REFN} to V_{REFP}) and the output power is evaluated as $20 \log(Amplitude)$ not $20 \log RMS$ so its value is -6 dB.
- The V_{SAH} is inverted as the input terminals V_{inp} and V_{inn} are reversed.
- The parasitic caps C_p values are not given so I put them 8 fF.